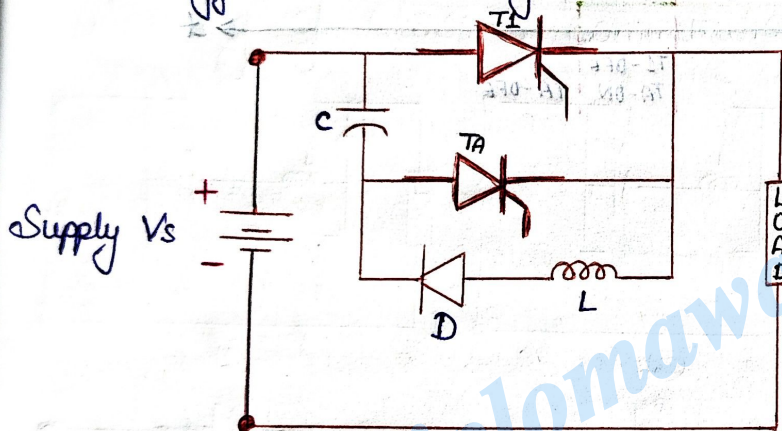


# Unit → 3

## 1.) Auxiliary Commutation... (Class D)


- It is also referred as Voltage commutation or Class D commutation. / Parallel Capacitor Commutation.
- In this method of commutation, a reverse voltage is suddenly applied across the thyristor, to turn it off. So, it is also known as voltage commutator.
- This type of commutation is also known as auxiliary commutation, as an auxiliary thyristor  $T_A$  is used to turn off the main thyristor  $T_M$ .





### Assumption

- Load current is constant.
- C is initially charged by  $V_s$ .

### \* Working of Class D Commutation...

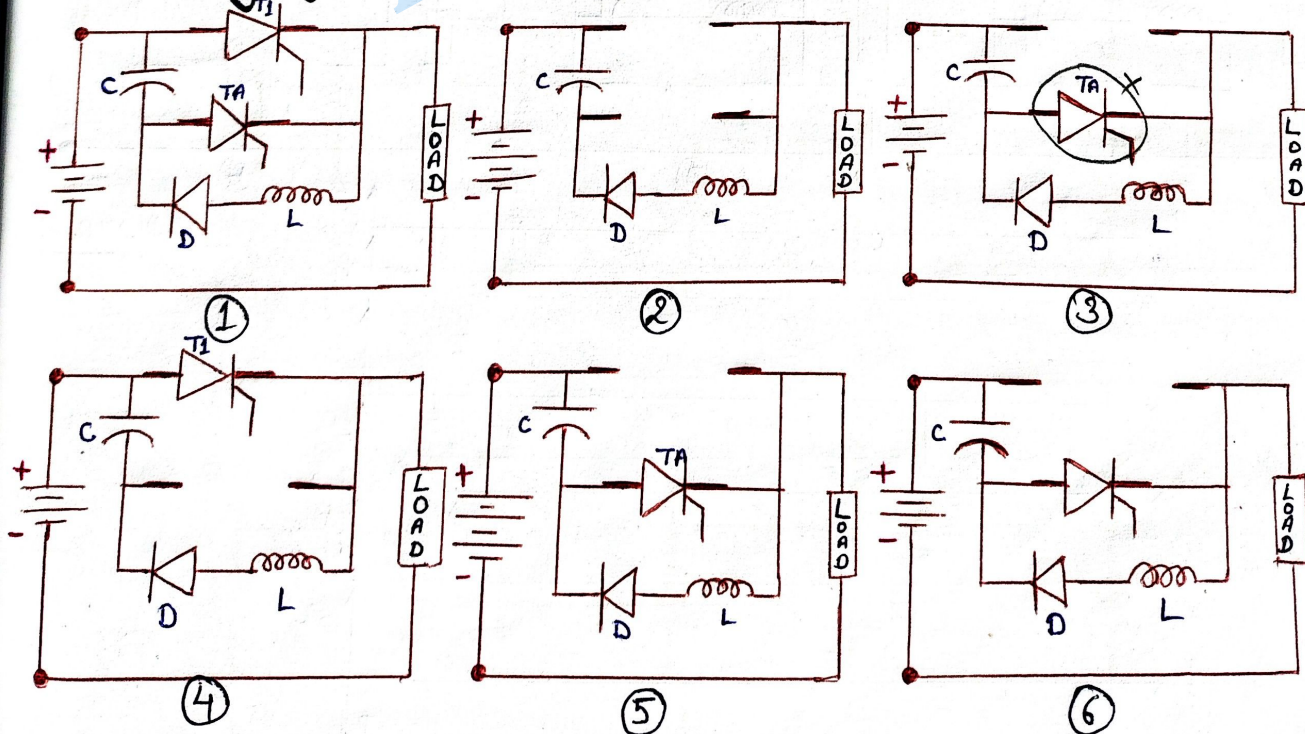

Waveform

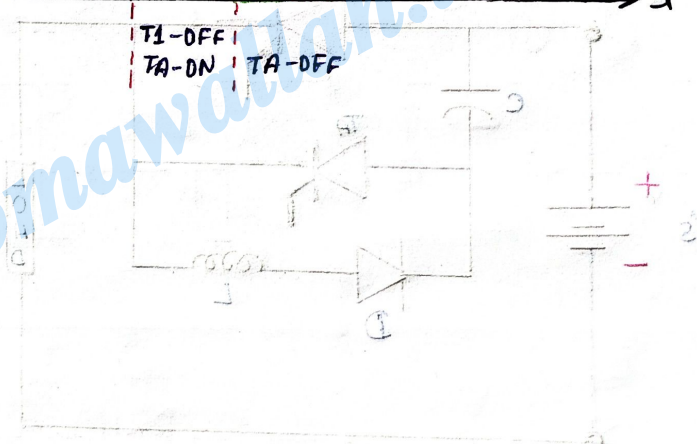
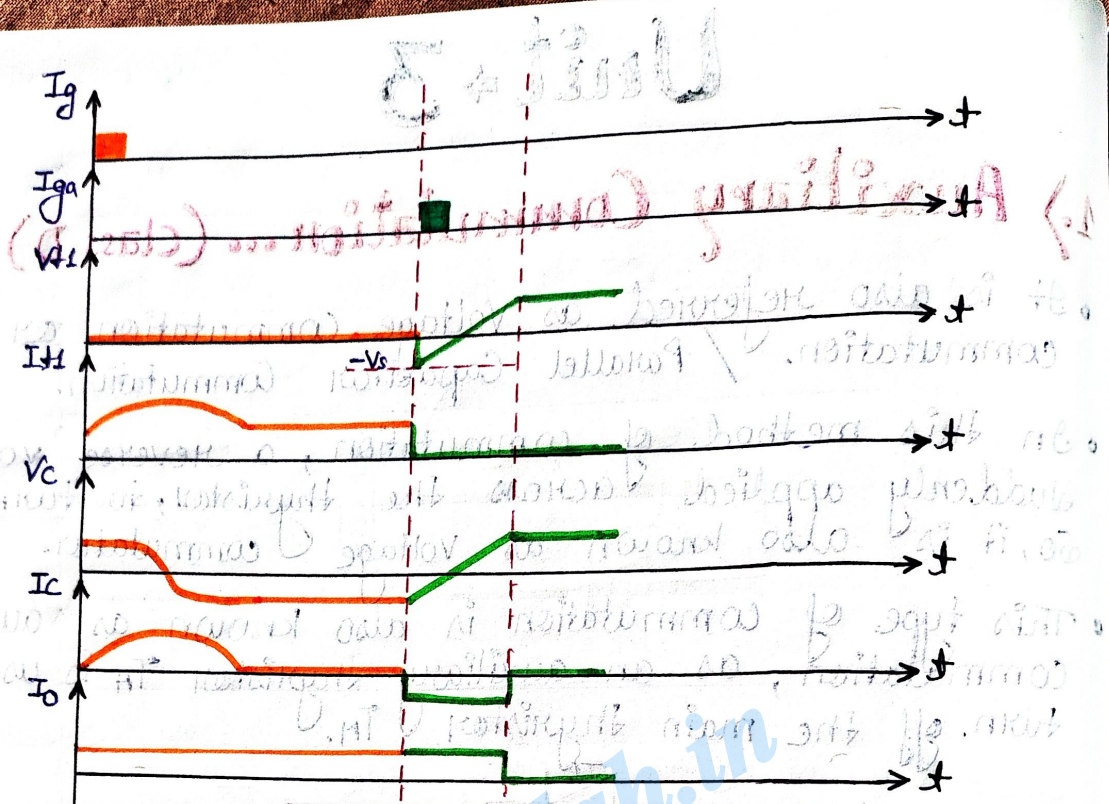


Working of Class B Comutation



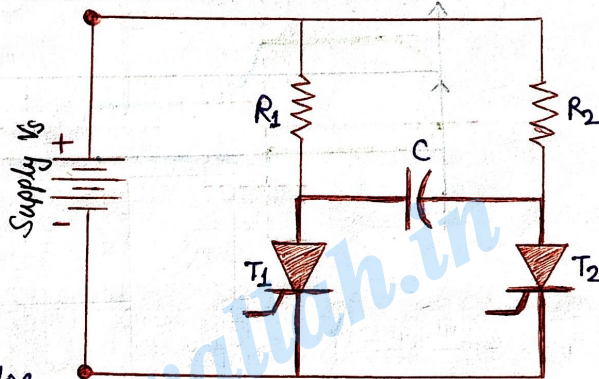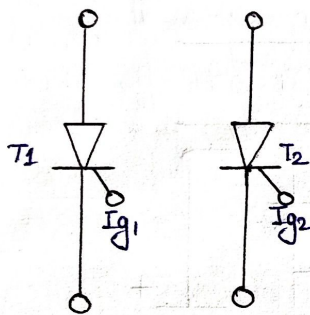
# # Complementary Commutation... (class c).

- It is also referred as impulse commutation or class c commutation.
- In this technique two thyristors are used for carrying the load current alternately.
- One thyristor is turned-off by turning on the other thyristor. The load current also ~~transfer~~ transfers from the outgoing thyristor to incoming thyristor.




To turn OFF SCR T<sub>1</sub>. gate pulse is given to SCR T<sub>2</sub>.  
 To turn OFF SCR T<sub>2</sub>. gate pulse is given to SCR T<sub>1</sub>.

## ★ Working of Class C Commutation

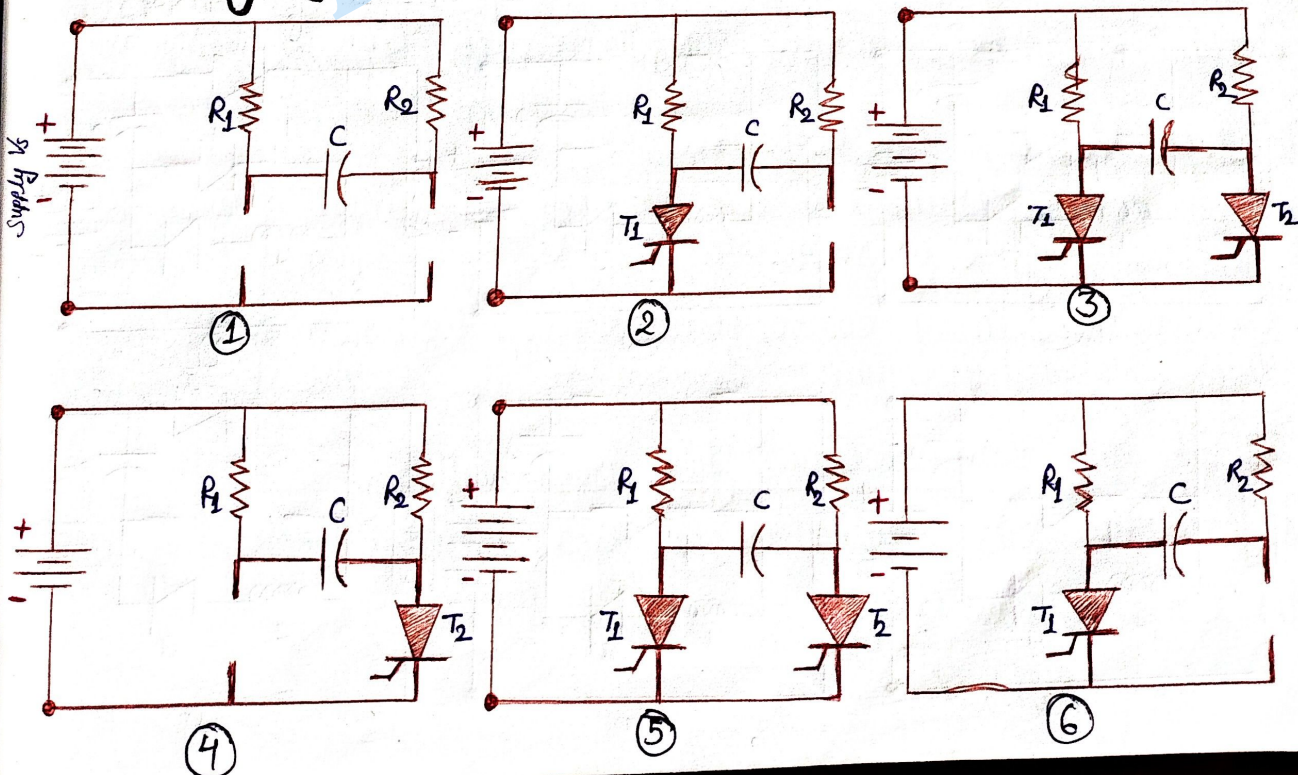

# Waveform

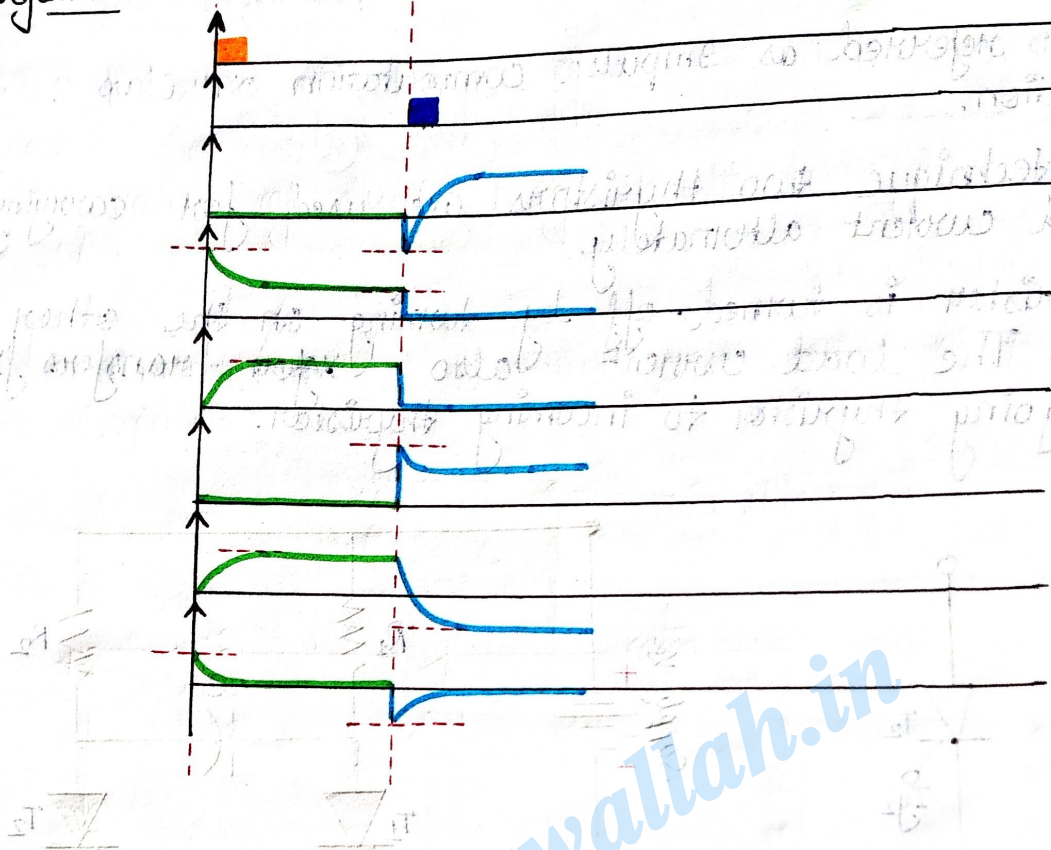

Diplomawallah.in

Working of Class C Comutation



## 2) Protection of SCR...


For satisfactory and reliable operation of thyristor, we need to protect it from various abnormal condition.

A thyristor must be provided following protection, in order to obtain reliable operation.

- (i)  $\frac{di}{dt}$  protection
- (ii)  $\frac{dv}{dt}$  protection
- (iii) Over voltage protection
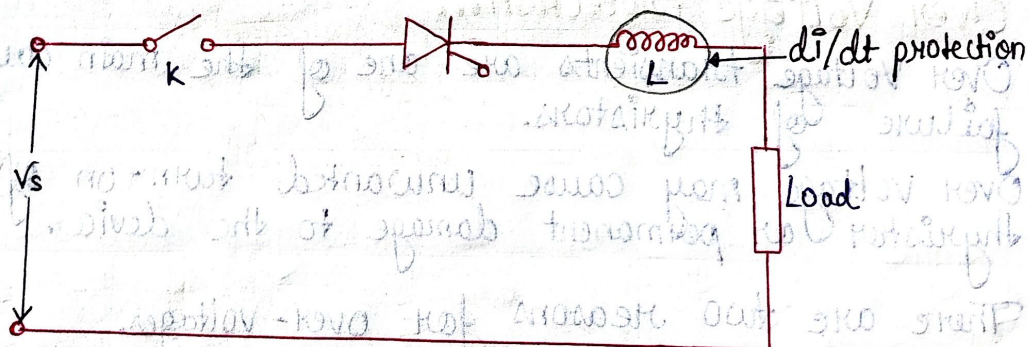
### # $\frac{di}{dt}$ protection...

- $di/dt$  is rate of change of current in device.
- When SCR is in forward bias, and it is ON by gate signal then, there will be flow of anode current.
- The anode current requires some time to spread inside device.
- $di/dt >$  spread velocity of charge. then it creates hot spot and that may damage SCR.
- So, to maintain  $di/dt$  through SCR, we connect inductor in series to the SCR.




- Voltage across inductor can be calculated by

$$V_s = L \frac{di}{dt} \Rightarrow L = \frac{V_s}{di/dt}$$

$$L > \frac{V_s}{di/dt}$$
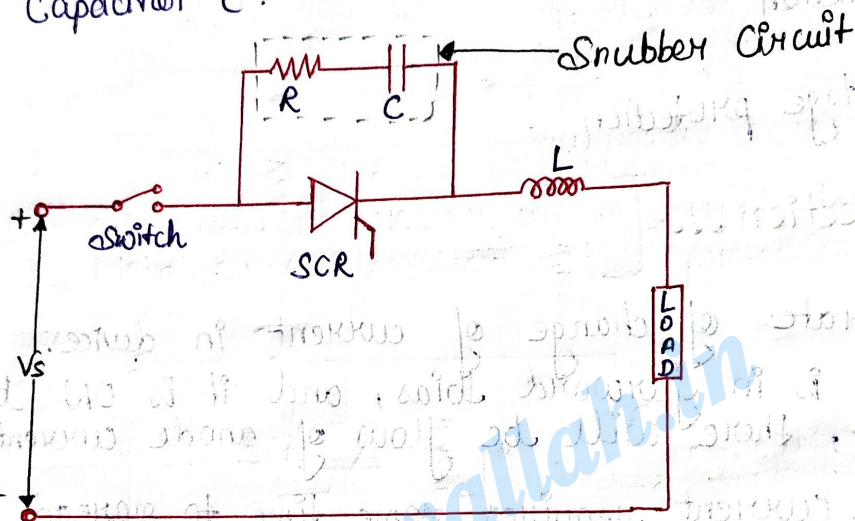
## # $\frac{dv}{dt}$ protection...

- $\frac{dv}{dt}$  is rate of change of voltage with respect to time.
- Higher value of  $\frac{dv}{dt}$  may result into false turn ON of SCR.
- To provide  $\frac{dv}{dt}$  protection we connect Snubber Circuit. The snubber circuit is a series combination of Resistor 'R' and Capacitor 'C'.



- Capacitor is connected to bypass high  $\frac{dv}{dt}$  through SCR.
- Resistor is connected to decrease discharge current of Capacitor through SCR.
- This R-C series across SCR is called Snubber circuit.

## # Over Voltage Protection...

- Over Voltage transients are one of the main causes of failure of thyristors.
- Over voltage may cause unwanted turn-on of a thyristor or permanent damage to the device.

There are two reasons for over-voltages.

- (i) Internal cause for over voltages.
- (ii) External causes of over voltages.

12/10/21

### (i) Internal causes of over-voltages.

Over voltage generated during commutation of a thyristor.  
Large  $\downarrow$   $di/dt$  during commutation, causes large transient voltage  $L \frac{di}{dt}$ .

### (ii) External causes of over-voltages.

- Due to interruption of current in an inductive circuit.
- Due to lightning stroke on feeder lines.
- Due to energizing or de-energizing of primary of transformer connected in the circuit.

\* Over voltage protection of thyristor is achieved by use of:-

- (a) Voltage Snubber circuit or RC circuits.
- (b) Voltage Clamping device or Non-Linear Resistors.

#### (a) Use of Snubber circuit or RC circuit...

- Voltage snubber circuit or RC circuit is connected across the device to be protected.
- Snubber circuit provide two protection.
  - ↳ Large voltage protection
  - ↳  $\frac{dv}{dt}$  protection.
- Snubber circuit provides a local path for reverse recovery current, thus reducing internal over-voltages.

#### (b) Use of Voltage-clamping device or Non-linear resistor...

- A voltage-clamping device is a non-linear resistor. It is also known as varistor.
- For a non-linear resistor, resistance value decreases with increasing voltage.
- So, a non-linear resistor or varistor is connected across SCR to protect it from over voltage.


Under normal condition

↳ voltage is within limits  $\Rightarrow$  so, resistance is high  
 $\Downarrow$   
so, it only allow very small current.

When over-voltage occurs



↳ when surge voltage appears  $\Rightarrow$  the device resistance decreases  
 $\Downarrow$   
it almost create a short-circuit path across SCR.  
The only a small voltage appears across SCR.

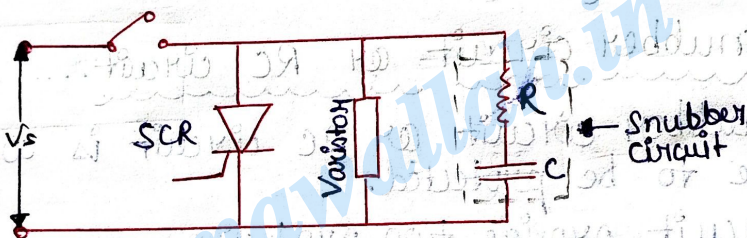Example :- Selenium thyrector diodes } used for over-voltage protection of SCR.  
Metal oxides varistors



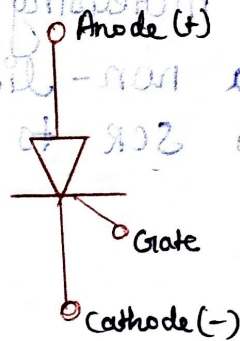
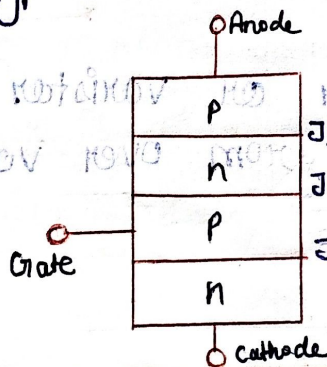
### 3.) Controlled rectifiers ... (SCR) Thyristor

- The word thyristor is derived by a combination of the THYRatron and tranSTOR, which means that thyristor is a solid state device like transistor and has a characteristics similar to that of the thyatron tube.
- SCR is one of the semi-conductor device in thyristor family.
- Silicon Controlled Rectifier is four layers of alternate p-type and n-type semiconductors forming three junctions  $J_1, J_2$  and  $J_3$ .



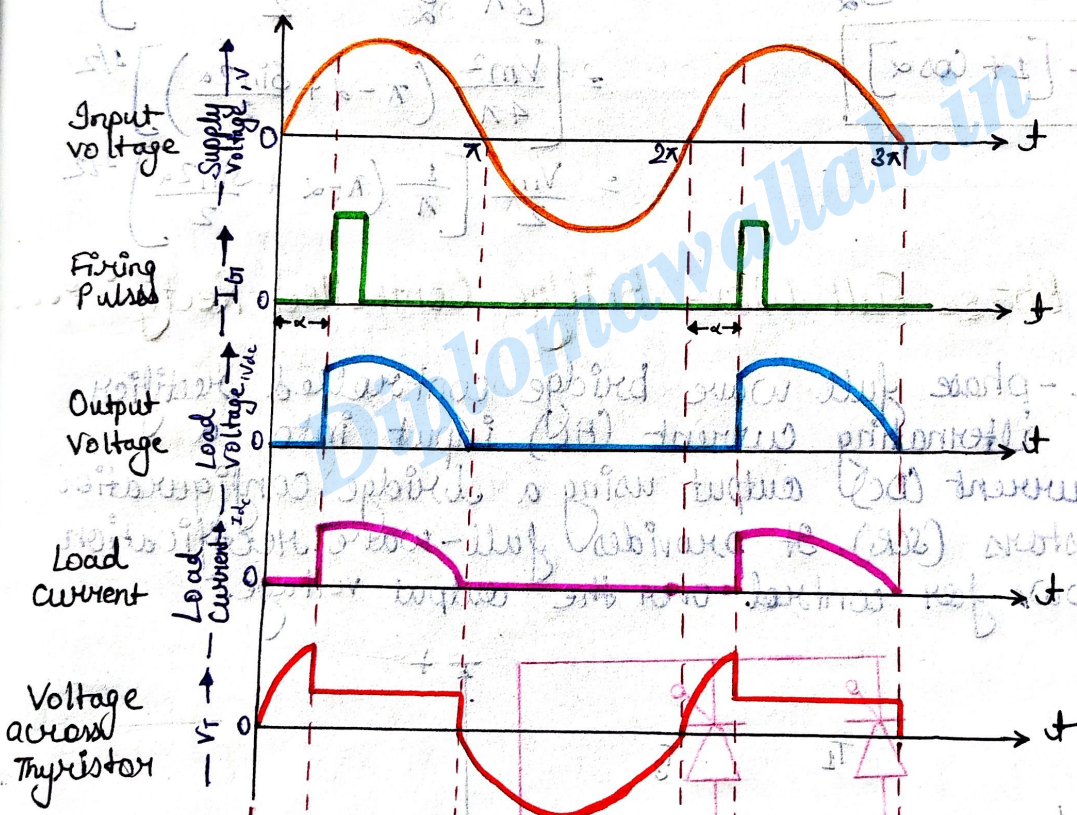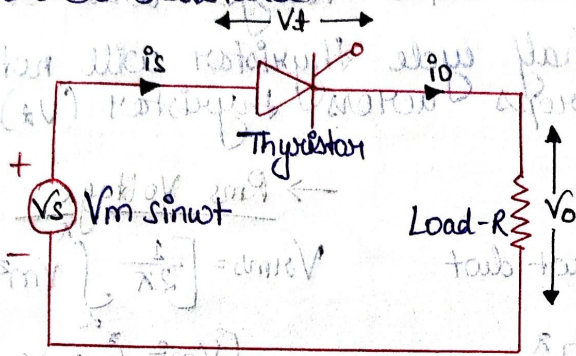
# # Single Phase Half-Wave Controlled Rectifier

- Single phase half wave controlled rectifier is a type of thyristor circuit that generates the output voltage in positive half cycle of supply.
- This is circuit diagram which consist of source voltage, thyristor, load resistance.


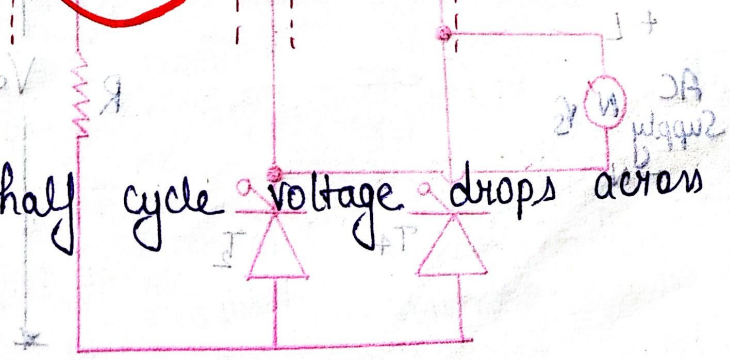
## Working :-

- During positive half cycle a voltage drops across thyristor i.e.  $V_t$ .



- When voltage drops at that time thyristor don't work due to lack of gate triggering.
- When we applied gate pulse by an get terminal then thyristor comes in working state and current starts to flow across thyristor.  $I_{io}$  is the no load current.
- This is output current ( $i_o$ ) will flow across load resistance ( $R$ ) and output voltage will be ( $V_o$ ).
- During negative half cycle thyristor will not conduct across thyristor ( $V^+$ ).

→ DC Voltage

$$V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$

$$V_{dc} = \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi}$$

$$V_{dc} = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

→ Rms Voltage

$$V_{rms} = \left[ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d\omega t \right]^{1/2}$$


$$= \left[ \frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} \, d\omega t \right]^{1/2}$$


$$= \left[ \frac{V_m^2}{4\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$

$$= \frac{V_m}{2} \left[ \frac{1}{\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$
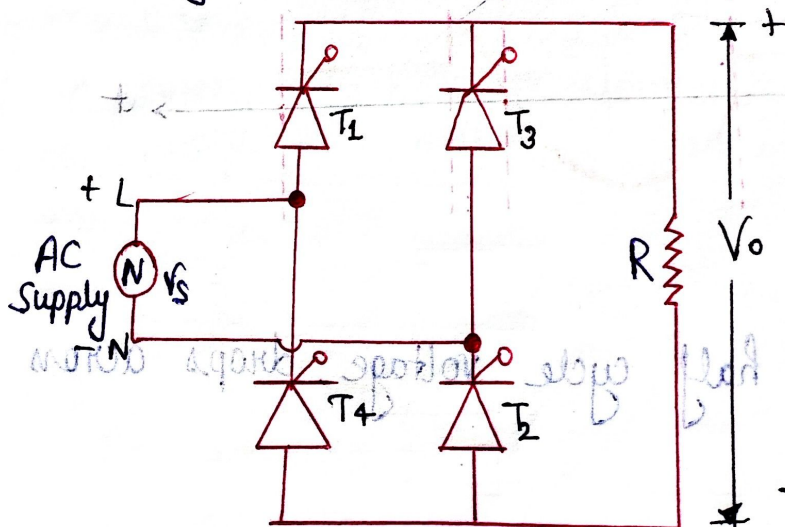
## # Single Phase Full Wave Bridge Controlled Rectifier...

- A single-phase full wave bridge controlled rectifier converts alternating current (AC) input into a direct current (DC) output using a bridge configuration of thyristors (SCR). It provides full-wave rectification and allows for control over the output voltage.



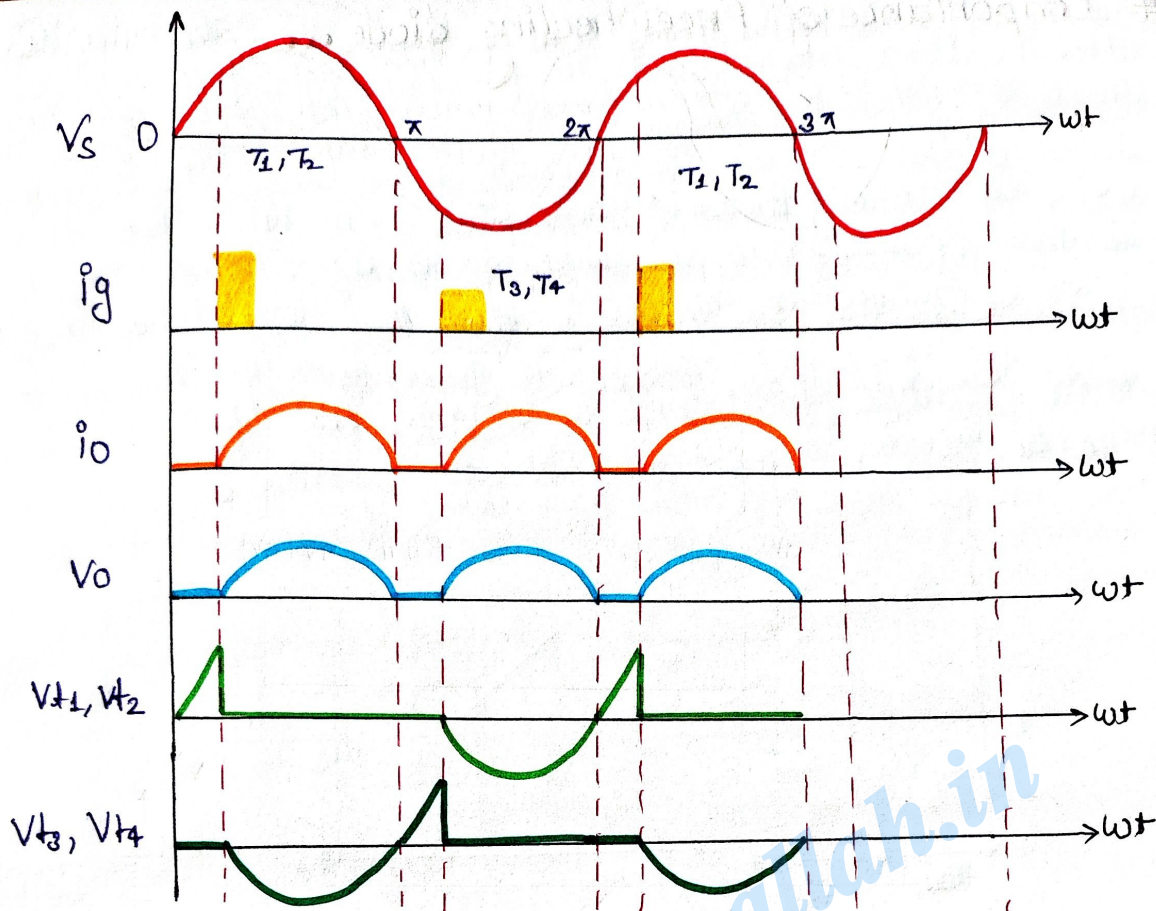

### Working -

- During the first positive half cycle, thyristor  $T_1$  and  $T_2$  are forward biased and if they are triggered simultaneously, the current flows through the load via thyristor  $T_1$ -load- $T_2$ -source. Thus, during positive half cycle, thyristor  $T_1$  and  $T_2$  are conducting.
- During negative half cycle of the ac input, thyristor  $T_3$  and  $T_4$  are forward biased and if they are triggered simultaneously, the current flows through the load via thyristor  $T_3$ -load- $T_4$ -source.
- Thyristors  $T_1, T_3$  and  $T_2, T_4$  are triggered at the same firing angle  $\alpha$  in each positive and negative half cycles of the supply voltage respectively.
- When the supply voltage falls to zero. Thus thyristors  $T_1, T_2$  in positive half cycle and  $T_3$  and  $T_4$  in negative half cycle turn off by natural commutation.